



- [Table of Contents](#)

Signal Integrity - Simplified

By [Eric Bogatin](#)

[Start Reading ▶](#)

Publisher: Prentice Hall PTR

Pub Date: September 15, 2003

ISBN: 0-13-066946-6

Pages: 608

[Copyright](#)

[Prentice Hall Modern Semiconductor Design Series](#)

[About Prentice Hall Professional Technical Reference](#)

[Preface](#)

[Top Ten Signal Integrity Principles](#)

[Chapter 1. Signal Integrity Is in Your Future](#)

[Section 1.1. What Is Signal Integrity?](#)

[Section 1.2. Signal Quality on a Single Net](#)

[Section 1.3. Cross Talk](#)

[Section 1.4. Rail-Collapse Noise](#)

[Section 1.5. Electromagnetic Interference \(EMI\)](#)

[Section 1.6. Two Important Signal Integrity Generalizations](#)

[Section 1.7. Trends in Electronic Products](#)

[Section 1.8. The Need for a New Design Methodology](#)

[Section 1.9. A New Product Design Methodology](#)

[Section 1.10. Simulations](#)

[Section 1.11. Modeling and Models](#)

[Section 1.12. Creating Circuit Models from Calculation](#)

[Section 1.13. Three Types of Measurements](#)

[Section 1.14. The Role of Measurements](#)

[Section 1.15. The Bottom Line](#)

[Chapter 2. Time and Frequency Domains](#)

[Section 2.1. The Time Domain](#)

[Section 2.2. Sine Waves in the Frequency Domain](#)

[Section 2.3. Shorter Time to a Solution in the Frequency Domain](#)

[Section 2.4. Sine Wave Features](#)

[Section 2.5. The Fourier Transform](#)

[Section 2.6. The Spectrum of a Repetitive Signal](#)

[Section 2.7. The Spectrum of an Ideal Square Wave](#)

[Section 2.8. From the Frequency Domain to the Time Domain](#)

[Section 2.9. Effect of Bandwidth on Rise Time](#)

[Section 2.10. Bandwidth and Rise Time](#)

[Section 2.11. What Does "Significant" Mean?](#)

[Section 2.12. Bandwidth of Real Signals](#)

[Section 2.13. Bandwidth and Clock Frequency](#)

[Section 2.14. Bandwidth of a Measurement](#)

[Section 2.15. Bandwidth of a Model](#)

[Section 2.16. Bandwidth of an Interconnect](#)

[Section 2.17. Bottom Line](#)

[Chapter 3. Impedance and Electrical Models](#)

[Section 3.1. Describing Signal-Integrity Solutions in Terms of Impedance](#)

[Section 3.2. What Is Impedance?](#)

[Section 3.3. Real vs. Ideal Circuit Elements](#)

[Section 3.4. Impedance of an Ideal Resistor in the Time Domain](#)

[Section 3.5. Impedance of an Ideal Capacitor in the Time Domain](#)

[Section 3.6. Impedance of an Ideal Inductor in the Time Domain](#)

[Section 3.7. Impedance in the Frequency Domain](#)

[Section 3.8. Equivalent Electrical Circuit Models](#)

[Section 3.9. Circuit Theory and SPICE](#)

[Section 3.10. Introduction to Modeling](#)

[Section 3.11. The Bottom Line](#)

[Chapter 4. The Physical Basis of Resistance](#)

[Section 4.1. Translating Physical Design into Electrical Performance](#)

[Section 4.2. The Only Good Approximation for the Resistance of Interconnects](#)

[Section 4.3. Bulk Resistivity](#)

[Section 4.4. Resistance per Length](#)

[Section 4.5. Sheet Resistance](#)

[Section 4.6. The Bottom Line](#)

[Chapter 5. The Physical Basis of Capacitance](#)

[Section 5.1. Current Flow in Capacitors](#)

[Section 5.2. The Capacitance of a Sphere](#)

[Section 5.3. Parallel Plate Approximation](#)

[Section 5.4. Dielectric Constant](#)

[Section 5.5. Power and Ground Planes and Decoupling Capacitance](#)

[Section 5.6. Capacitance per Length](#)

[Section 5.7. 2D Field Solvers](#)

[Section 5.8. Effective Dielectric Constant](#)

[Section 5.9. The Bottom Line](#)

[Chapter 6. The Physical Basis of Inductance](#)

[Section 6.1. What Is Inductance?](#)

[Section 6.2. Inductance Principle #1: There Are Circular Magnetic-Field Line Loops Around All Currents](#)

[Section 6.3. Inductance Principle #2: Inductance Is the Number of Webers of Field Line Loops Around a Conductor per Amp of Current Through It](#)

[Section 6.4. Self-Inductance and Mutual Inductance](#)

[Section 6.5. Inductance Principle #3: When the Number of Field Line Loops Around a Conductor Changes, There Will Be a Voltage Induced Across the Ends of the Conductor](#)

[Section 6.6. Partial Inductance](#)

[Section 6.7. Effective, Total, or Net Inductance and Ground Bounce](#)

[Section 6.8. Loop Self- and Mutual Inductance](#)

[Section 6.9. The Power-Distribution System \(PDS\) and Loop Inductance](#)

[Section 6.10. Loop Inductance per Square of Planes](#)

[Section 6.11. Loop Inductance of Planes and Via Contacts](#)

[Section 6.12. Loop Inductance of Planes with a Field of Clearance Holes](#)

[Section 6.13. Loop Mutual Inductance](#)

[Section 6.14. Equivalent Inductance](#)

- [Section 6.15. Summary of Inductance](#)
- [Section 6.16. Current Distributions and Skin Depth](#)
- [Section 6.17. High-Permeability Materials](#)
- [Section 6.18. Eddy Currents](#)
- [Section 6.19. The Bottom Line](#)

[Chapter 7. The Physical Basis of Transmission Lines](#)

- [Section 7.1. Forget the Word *Ground*](#)
- [Section 7.2. The Signal](#)
- [Section 7.3. Uniform Transmission Lines](#)
- [Section 7.4. The Speed of Electrons in Copper](#)
- [Section 7.5. The Speed of a Signal in a Transmission Line](#)
- [Section 7.6. Spatial Extent of the Leading Edge](#)
- [Section 7.7. "Be the Signal"](#)
- [Section 7.8. The Instantaneous Impedance of a Transmission Line](#)
- [Section 7.9. Characteristic Impedance and Controlled Impedance](#)
- [Section 7.10. Famous Characteristic Impedances](#)
- [Section 7.11. *The* Impedance of a Transmission Line](#)
- [Section 7.12. Driving a Transmission Line](#)
- [Section 7.13. Return Paths](#)
- [Section 7.14. When Return Paths Switch Reference Planes](#)
- [Section 7.15. A First-Order Model of a Transmission Line](#)
- [Section 7.16. Calculating Characteristic Impedance with Approximations](#)
- [Section 7.17. Calculating the Characteristic Impedance with a 2D Field Solver](#)
- [Section 7.18. An n-Section Lumped Circuit Model](#)
- [Section 7.19. Frequency Variation of the Characteristic Impedance](#)
- [Section 7.20. The Bottom Line](#)

[Chapter 8. Transmission Lines and Reflections](#)

- [Section 8.1. Reflections at Impedance Changes](#)
- [Section 8.2. Why Are There Reflections?](#)
- [Section 8.3. Reflections from Resistive Loads](#)
- [Section 8.4. Source Impedance](#)
- [Section 8.5. Bounce Diagrams](#)
- [Section 8.6. Simulating Reflected Waveforms](#)
- [Section 8.7. Measuring Reflections with a TDR](#)
- [Section 8.8. Transmission Lines and Unintentional Discontinuities](#)
- [Section 8.9. When to Terminate](#)
- [Section 8.10. The Most Common Termination Strategy for Point-to-Point Topology](#)
- [Section 8.11. Reflections from Short Series Transmission Lines](#)
- [Section 8.12. Reflections from Short-Stub Transmission Lines](#)
- [Section 8.13. Reflections from Capacitive End Terminations](#)
- [Section 8.14. Reflections from Capacitive Loads in the Middle of a Trace](#)
- [Section 8.15. Capacitive Delay Adders](#)
- [Section 8.16. Effects of Corners and Vias](#)
- [Section 8.17. Loaded Lines](#)
- [Section 8.18. Reflections from Inductive Discontinuities](#)
- [Section 8.19. Compensation](#)
- [Section 8.20. The Bottom Line](#)

[Chapter 9. Lossy Lines, Rise-Time Degradation, and Material Properties](#)

- [Section 9.1. Why Worry About Lossy Lines](#)
- [Section 9.2. Losses in Transmission Lines](#)
- [Section 9.3. Sources of Loss: Conductor Resistance and Skin Depth](#)
- [Section 9.4. Sources of Loss: The Dielectric](#)
- [Section 9.5. Dissipation Factor](#)
- [Section 9.6. The Real Meaning of Dissipation Factor](#)

[Section 9.7. Modeling Lossy Transmission Lines](#)
[Section 9.8. Characteristic Impedance of a Lossy Transmission Line](#)
[Section 9.9. Signal Velocity in a Lossy Transmission Line](#)
[Section 9.10. Attenuation and the dB](#)
[Section 9.11. Attenuation in Lossy Lines](#)
[Section 9.12. Measured Properties of a Lossy Line in the Frequency Domain](#)
[Section 9.13. The Bandwidth of an Interconnect](#)
[Section 9.14. Time-Domain Behavior of Lossy Lines](#)
[Section 9.15. Improving the Eye Diagram of a Transmission Line](#)
[Section 9.16. Pre-emphasis and Equalization](#)
[Section 9.17. The Bottom Line](#)

[Chapter 10. Cross Talk in Transmission Lines](#)

[Section 10.1. Superposition](#)
[Section 10.2. Origin of Coupling: Capacitance and Inductance](#)
[Section 10.3. Cross Talk in Transmission Lines: NEXT and FEXT](#)
[Section 10.4. Describing Cross Talk](#)
[Section 10.5. The SPICE Capacitance Matrix](#)
[Section 10.6. The Maxwell Capacitance Matrix and 2D Field Solvers](#)
[Section 10.7. The Inductance Matrix](#)
[Section 10.8. Cross Talk in Uniform Transmission Lines and Saturation Length](#)
[Section 10.9. Capacitively Coupled Currents](#)
[Section 10.10. Inductively Coupled Currents](#)
[Section 10.11. Near-End Cross Talk](#)
[Section 10.12. Far-End Cross Talk](#)
[Section 10.13. Decreasing Far-End Cross Talk](#)
[Section 10.14. Simulating Cross Talk](#)
[Section 10.15. Guard Traces](#)
[Section 10.16. Cross Talk and Dielectric Constant](#)
[Section 10.17. Cross Talk and Timing](#)
[Section 10.18. Switching Noise](#)
[Section 10.19. Summary of Reducing Cross Talk](#)
[Section 10.20. The Bottom Line](#)

[Chapter 11. Differential Pairs and Differential Impedance](#)

[Section 11.1. Differential Signaling](#)
[Section 11.2. A Differential Pair](#)
[Section 11.3. Differential Impedance with No Coupling](#)
[Section 11.4. The Impact from Coupling](#)
[Section 11.5. Calculating Differential Impedance](#)
[Section 11.6. The Return-Current Distribution in a Differential Pair](#)
[Section 11.7. Odd and Even Modes](#)
[Section 11.8. Differential Impedance and Odd-Mode Impedance](#)
[Section 11.9. Common Impedance and Even-Mode Impedance](#)
[Section 11.10. Differential and Common Signals and Odd- and Even-Mode Voltage Components](#)
[Section 11.11. Velocity of Each Mode and Far-End Cross Talk](#)
[Section 11.12. Ideal Coupled Transmission-Line Model or an Ideal Differential Pair](#)
[Section 11.13. Measuring Even- and Odd-Mode Impedance](#)
[Section 11.14. Terminating Differential and Common Signals](#)
[Section 11.15. Conversion of Differential to Common Signals](#)
[Section 11.16. EMI and Common Signals](#)
[Section 11.17. Cross Talk in Differential Pairs](#)
[Section 11.18. Crossing a Gap in the Return Path](#)
[Section 11.19. To Tightly Couple or Not to Tightly Couple](#)
[Section 11.20. Calculating Odd and Even Modes from Capacitance- and Inductance-Matrix Elements](#)
[Section 11.21. The Characteristic Impedance Matrix](#)

[Section 11.22. The Bottom Line](#)

[Appendix A. 100 General Design Guidelines to Minimize Signal-Integrity Problems](#)

[Section A.1. Minimize Signal-Quality Problems on One Net](#)

[Section A.2. Minimize Cross Talk](#)

[Section A.3. Minimize Rail Collapse](#)

[Section A.4. Minimize EMI](#)

[Appendix B. 100 Collected Rules of Thumb to Help Estimate Signal-Integrity Effects](#)

[Section B.1. Chapter 2](#)

[Section B.2. Chapter 3](#)

[Section B.3. Chapter 4](#)

[Section B.4. Chapter 5](#)

[Section B.5. Chapter 6](#)

[Section B.6. Chapter 7](#)

[Section B.7. Chapter 8](#)

[Section B.8. Chapter 9](#)

[Section B.9. Chapter 10](#)

[Section B.10. Chapter 11](#)

[Appendix C. Selected References](#)

[About the Author](#)

[[Team LiB](#)]

